


Problem 1

$$d = gh + p$$


$$p = N = 2$$

$$g = \frac{42N}{3} = \frac{5}{3}$$

$$d = \frac{5}{3}h + 2$$

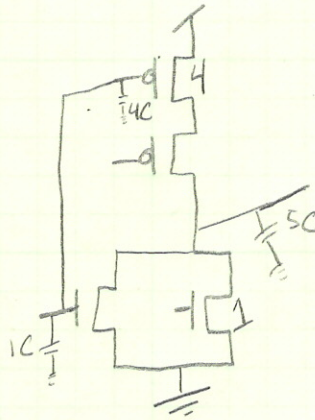


$$shC shR = 2sh^2 \text{ delay}$$

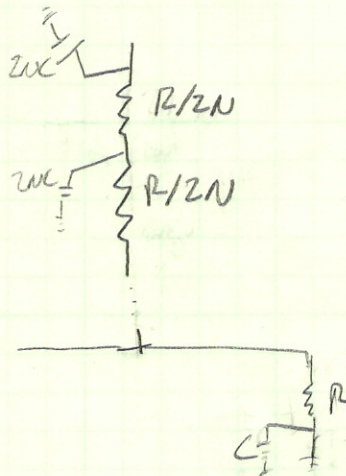Problem 2

$$R(C + N2NC) + \sum_{n=0}^{N-1} R_{in}(n2NC)$$

Problem 3

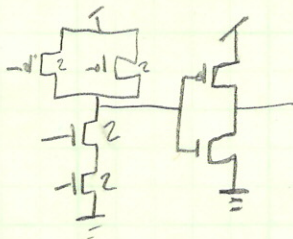
(a) will be faster because it will have less capacitance than (b)



$$d = gh + p \quad g = \frac{2+N/3}{4/3}, \quad p = \frac{N}{2}, \quad h = \frac{C_{in}}{C_{out}} = 1$$

$$d = \frac{4}{3} + 2 = \frac{10}{3} \text{ for NAND}$$

$$d = 1 \text{ for Inverter}$$

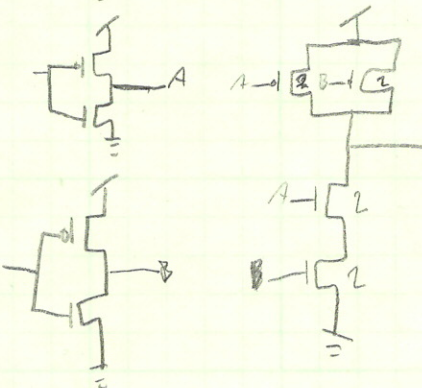


$$d = \frac{3+4}{3}(1) + 2 = \frac{7}{3} + 2 = \frac{13}{3} \text{ for NAND}$$

$$\text{delay (a)} = \frac{10}{3}$$


$$\text{delay (b)} = \frac{13}{3}$$

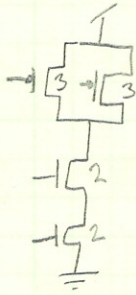Problem 4

logical effort = $g = \frac{C_t}{C_{in}} = \frac{C_t}{C_{in}}$ because equally sized



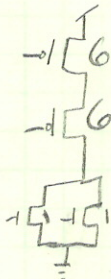
$$C_t = 5, C_{in} = 4 = \underline{\underline{\frac{5}{4} \text{ NAND}}}$$



$$C_t = 7, C_{in} = 4 = \underline{\underline{\frac{7}{4} \text{ NOR}}}$$

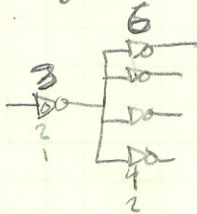Problem 5

There's not a lot of detail of what is going on. What we know: successively larger (how much larger?) FO4 (fanout of 4)



$$d = gh + p \quad d_0 = (1) \left(\frac{4 \cdot 6}{3} \right) + \frac{3}{3} = 8 + 1 = 9$$

$$d_1 = \left(\frac{6}{3} \right) h + \frac{6}{3} = 2h + 2 = 1002$$

$$load = \frac{10p}{208} = 500$$

Use as few inverters as possible, assuming FO4 use 5 inverters for a delay of 1011